

# CHAPTER 6

## **Bipolar Junction Transistors (BJTs)**

# Outlines

- 6.1 Device structure and physical operation
- 6.2 Current-voltage characteristics
- 6.3 BJT circuits at dc

# 6.1 Device structure and physical operation

- 6.2.1 Simplified structure and operations
  - NPN and PNP BJT


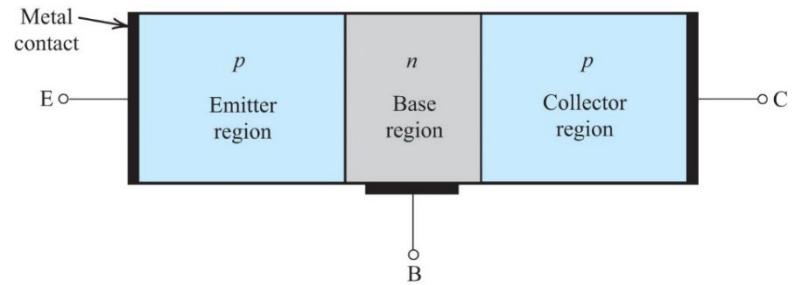
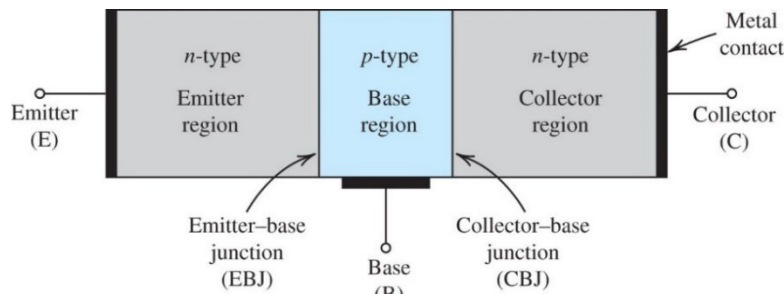
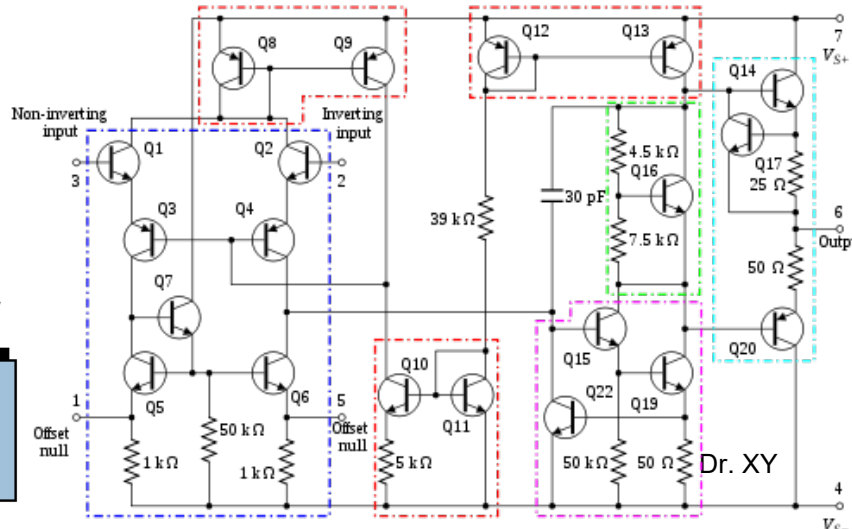


Figure 6.1 A simplified structure of the *npn* transistor.

Figure 6.2 A simplified structure of the *pnp* transistor.

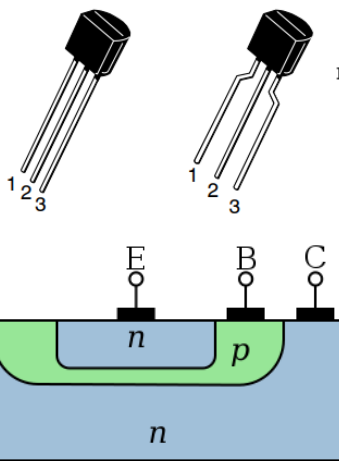


## • 6.2.1 Operational modes

- Cutoff region: There is no base current, so no collector or emitter current.
- Active region: Collector current is  $\beta \times$  base current. BE junction forward bias, or  $V_{BE} \approx 0.7V$
- Saturation region: The collector and emitter are, in effect, shorted together. The transistor behaves a short circuit


$$V_{BE} \approx 0.7V$$

**Table 6.1** BJT Modes of Operation


Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

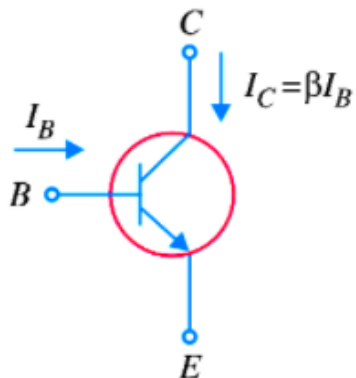

(i) ACTIVE

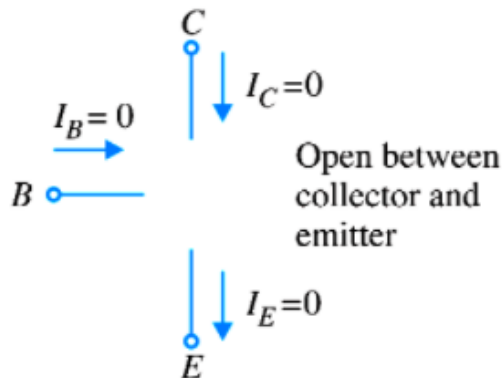

(ii) CUT-OFF

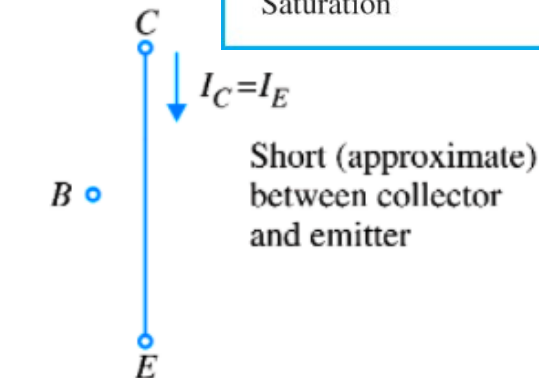

(iii) SATURATED

- 6.1.2 Operational Region of the NPN transistor

- $V_{BE}$  reverse bias: Cutoff
- $V_{BE}$  forward bias: Conducts


$$I_E = I_C + I_B; V_{BE} = 0.7V$$

- Active region:  $V_{BC}$  reverse bias ( $V_{BC} \leq 0.4V$ )

$$\rightarrow V_{CE} \geq 0.3V : I_C = \beta I_B$$

- Saturation region:  $V_{BC}$  forward bias ( $V_{BC} > 0.4V$ )
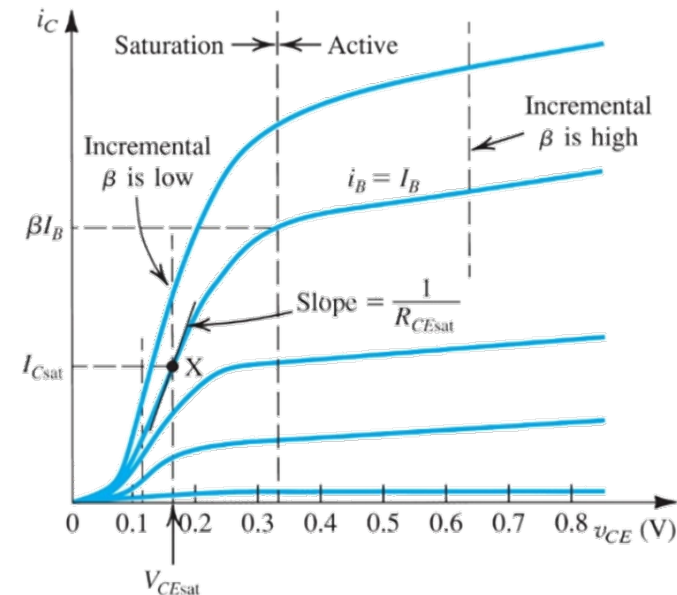
$$\rightarrow V_{CE} < 0.3V : I_C = \beta_{force} I_B$$



- 6.1.2 Operation in the active Region

$$I_C = \beta I_B \text{ or } I_B = \frac{I_C}{\beta},$$

- $\beta$ : Common-emitter current gain -- a transistor parameter (50~200)

$$I_E = I_C + I_B$$


- $I_E = \beta I_B + I_B = (\beta + 1)I_B$

- $I_E = I_C + \frac{I_C}{\beta} = \frac{\beta+1}{\beta} I_C$  or  $I_C = \frac{\beta}{\beta+1} I_E = \alpha I_E$


- $\alpha = \frac{\beta}{\beta+1}$  common base current gain

- 6.1.4 Operation in the saturation mode

$$\beta_{force} = \frac{I_C}{I_B} |_{saturation} \ll \beta$$

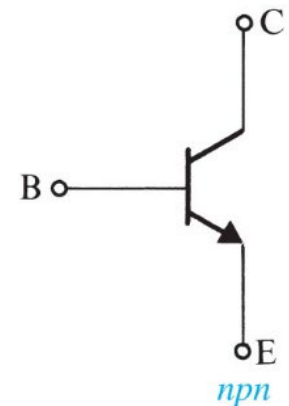


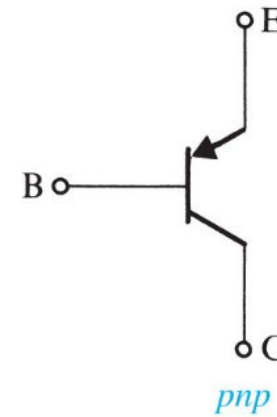- 6.1.5 Operation of the **PNP** transistor in the active mode
  - $V_{EB}$  makes EB forward bias,  $V_{CB}$  makes the CB reverse bias.
  - $I_E = I_C + I_B$ , ( $I_B$  current is leaving the transistor)
  - Difference:  $V_{BE} \Rightarrow V_{EB}$   $V_{CB} \Rightarrow V_{BC}$




# 6.2 Current-voltage characteristics

- 6.2.1 Circuit symbols and conventions
  - NPN active:
    - BE junction is forward-bias ( $V_{BE} \approx 0.7V$ )
    - CB junction is reverse-bias ( $V_C - V_B > -0.4V$ , or  $V_{CE} > 0.3V$ )
  - PNP active:
    - EB junction is forward-bias ( $V_{EB} \approx 0.7V$ )
    - BC junction is reverse-bias ( $V_B - V_C > -0.4V$ , or  $V_{EC} > 0.3V$ )

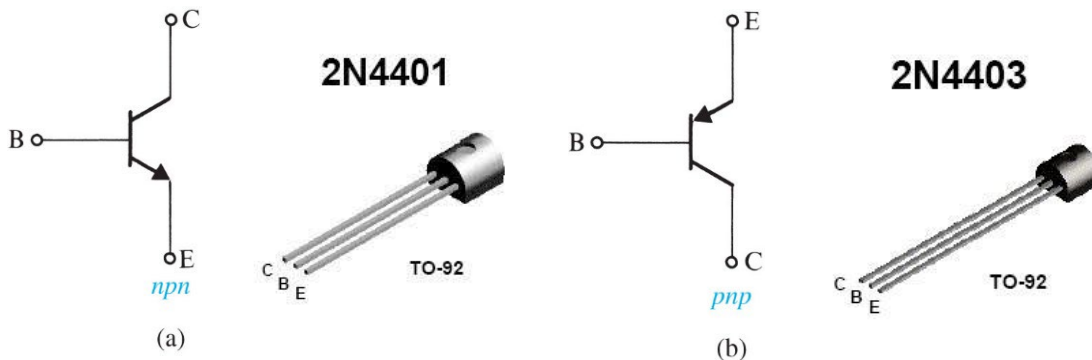

**Figure 6.12** Circuit symbols for BJTs.

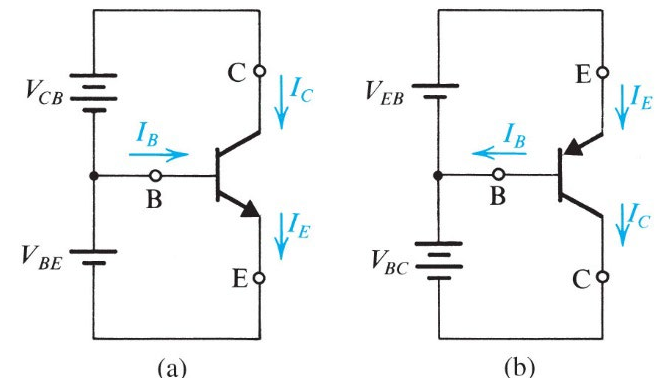

**Figure 6.13** Voltage polarities and current flow in transistors operating in the active mode.


# 6.2.4 An alternative form of the common-emitter characteristics

– Saturation region:

- $I_{Csat} = \beta_{forced} I_B$
- $\beta_{forced} < \beta$
- $V_{BE} \approx 0.7V$
- $V_{CEsat} < 0.3V$

Active-Saturation edge  $V_{CE} = 0.3V$

Deep saturation:  $V_{CE} = 0.2V$

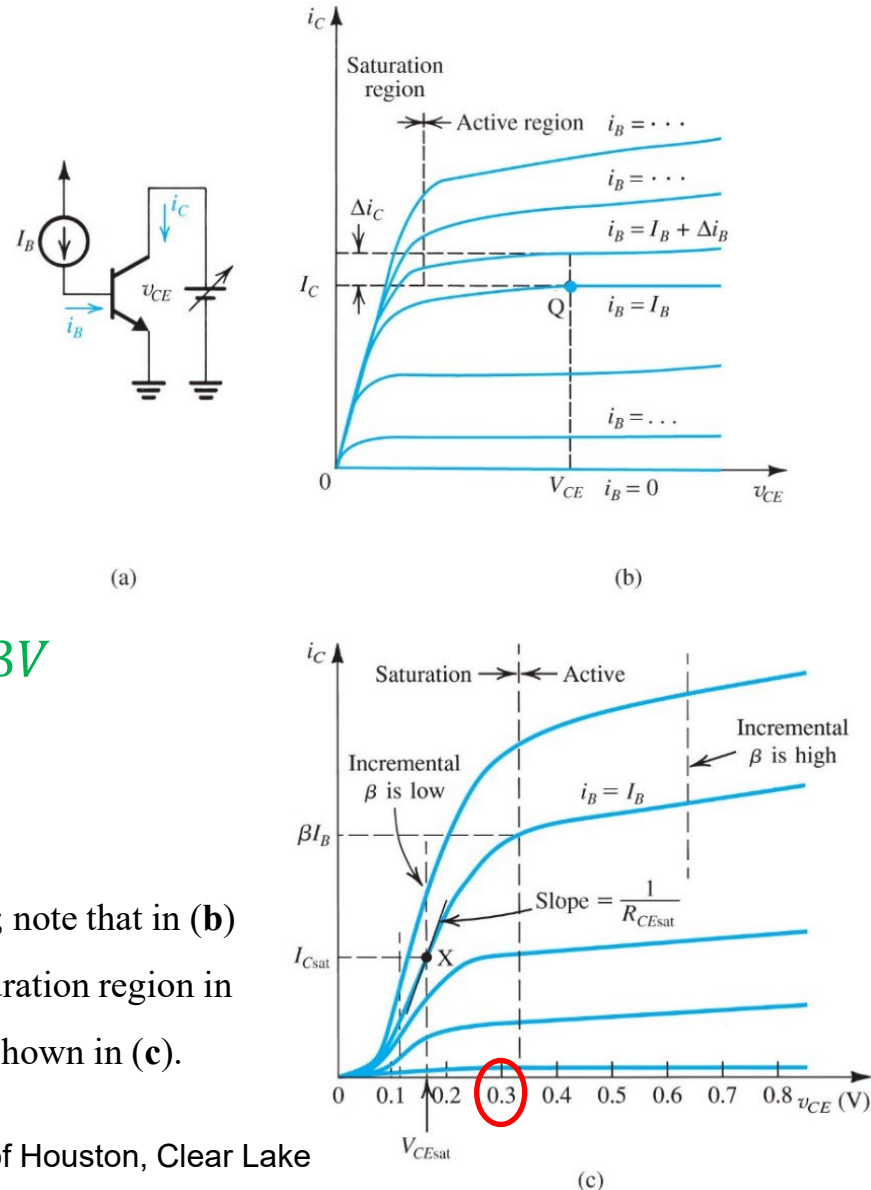

**Figure 6.20** Common-emitter characteristics. (a) Basic CE circuit; note that in (b) the horizontal scale is expanded around the origin to show the saturation region in some detail. A much greater expansion of the saturation region is shown in (c).

# • Example 6.3

$V_{BE} = 0.7V$  and  $\beta = 50$ . Find  $V_{BB}$  that results in the transistor operating

(a) In the active mode with  $V_{CE} = 5V$  (b) At the edge of saturation ( $V_{CE} = 0.3V$ )

(c) Deep in saturation ( $V_{CEsat} = 0.2V$ ) with  $\beta_{forced} = 10$

$$(a) I_C = \frac{V_{CC} - V_{CE}}{1} = \frac{10 - 5}{1} = 5mA$$

$$I_B = \frac{I_C}{\beta} = \frac{5}{50} = 0.1mA$$

$$V_{BB} = I_B \times R_B + V_{BE} = 0.1 \times 10 + 0.7 = 1.7V$$

$$(b) I_C = \frac{V_{CC} - V_{CE}}{1} = \frac{10 - 0.3}{1} = 9.7mA$$

$$I_B = \frac{I_C}{\beta} = \frac{9.7}{50} = 0.194mA$$

$$V_{BB} = I_B \times R_B + V_{BE} = 0.194 \times 10 + 0.7 = 2.64V$$

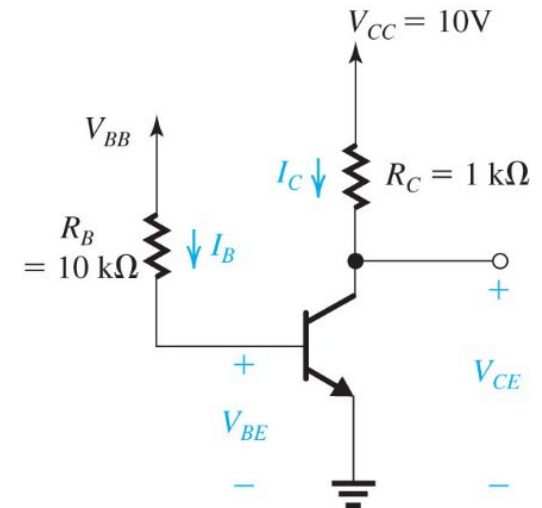


Figure 6.22 Circuit for Example 6.3.

## • Example 6.3

$V_{BE} = 0.7V$  and  $\beta = 50$ . Find  $V_{BB}$  that results in the transistor operating

(a) In the active mode with  $V_{CE} = 5V$  (b) At the edge of saturation ( $V_{CE} = 0.3V$ )

(c) Deep in saturation ( $V_{CEsat} = 0.2V$ ) with  $\beta_{forced} = 10$

$$(c) I_C = \frac{V_{CC} - V_{CEsat}}{1k\Omega} = \frac{10V - 0.2V}{1k\Omega} = 9.8mA$$

$$I_B = \frac{I_C}{\beta_{force}} = \frac{9.8mA}{10} = 0.98mA,$$

$$V_{BB} = I_B \times R_B + V_{BE} = 0.98mA \times 10k\Omega + 0.7V = 10.5V$$

In saturation region, increasing  $V_{BB}$  and thus  $I_B$  results in negligible change in  $I_C$  since  $V_{CEsat}$  changes only slightly.

Thus  $I_C$  is saturated!

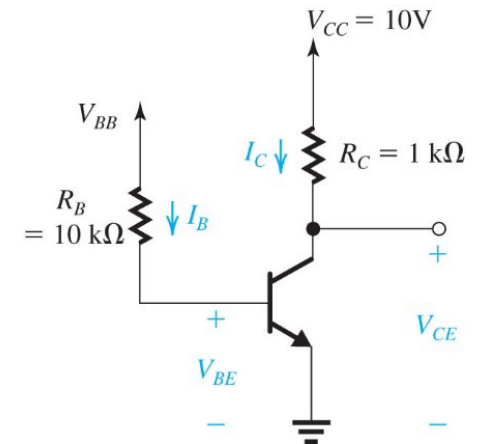



Figure 6.22 Circuit for Example 6.3.

# • Experiment 8.1

$V_{CC} = 10V, R_C = 1k\Omega .$

Find  $R_B$  for the following condition for when  $V_{CE} = 4V, 5V, \text{ and } 8V.$

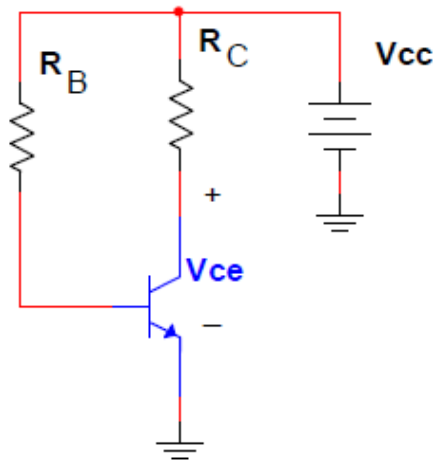Measure  $V_{CE}, V_{BE}, \text{ and } V_{CB}.$  In which region does the BJT operate for each corresponding  $R_B?$




$V_{CE} ?$	$R_B$	$V_{CE}$	$V_{BE}$	Region
4V				
5V				
8V				
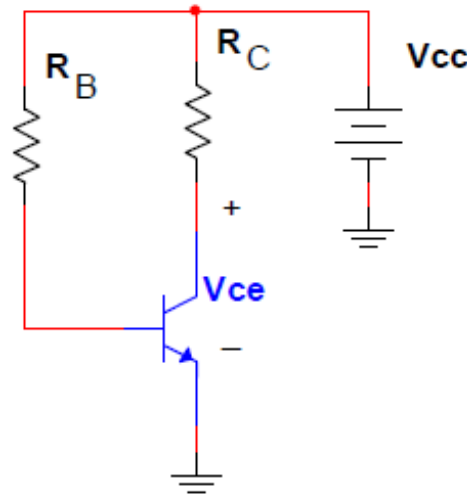
# • Experiment 8.2

$V_{CC} = 10V, R_C = R_B = 1k\Omega .$

Measure  $V_{CE}, V_{BE}$ , and  $V_{CB}$ . In which region does the BJT operate for corresponding  $R_B$ ?



$V_{CE}$	$V_{BE}$	Region

# 6.3 BJT circuits at dc

- In which mode is the transistor operating


**Top-Bottom (TB) rule: Top greater than bottom!**

– First TB (**EBJ**)?


- **T>B** ( $V_B > V_E$  for NPN and  $V_E > V_B$  for PNP)  $\Rightarrow$  Conducting ( $|V_{BE}| = 0.7V$ )
- **T<B**  $\Rightarrow$  **Cutoff**

– Second TB (**CBJ**)?

- **T>B** ( $V_{CE} > 0.3V$  for NPN and  $V_{EC} > 0.3V$  for PNP)  
 $\Rightarrow$  **Active** ( $I_C = \beta I_B$ )
- **T<B**  $\Rightarrow$  **Saturation** ( $|V_{CE}| = 0.2V, I_C = \beta_{forced} I_B$ )

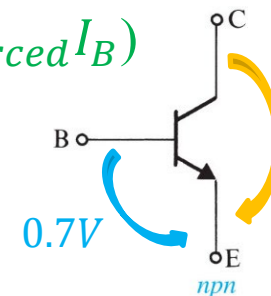

(a)

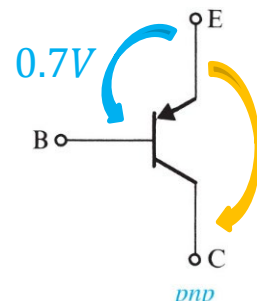

(b)

- Analysis procedure

- Find conduction ( $V_B$  VS.  $V_E$ : First TB rule)

- If conducting ( $|V_{BE}| = 0.7V$ ) -> assume in active mode first


- If not conducting, in cutoff

- Proceeds all currents and voltages

- Find active ( $V_C$  VS.  $V_B$ : Second TB rule)

- In active,  $I_C = \beta I_B$

- If not active, in saturation mode ( $|V_{CE}| = 0.2V$ ) -> redo the analysis

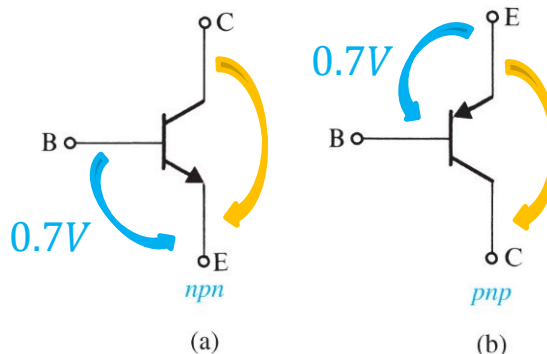

# • Example 6.4

Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents.

1) Glancing BE is forward bias ( $V_{BE} \approx 0.7V$ ), so the transistor conducts.

$$\text{KCL1: } 4 - 0.7 - I_E R_E = 0$$

$$I_E = \frac{3.3}{R_E} = 1mA$$


2) Assume in active mode.

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = 0.99mA$$

$$V_C = 10V - I_C R_C = 10 - 0.99 \times 4.7 = 5.3V$$

So  $V_{CE} = 2V > 0.3V$ , in active mode.

$$I_B = \frac{I_E}{1 + \beta} = \frac{1}{101} \approx 0.01mA$$

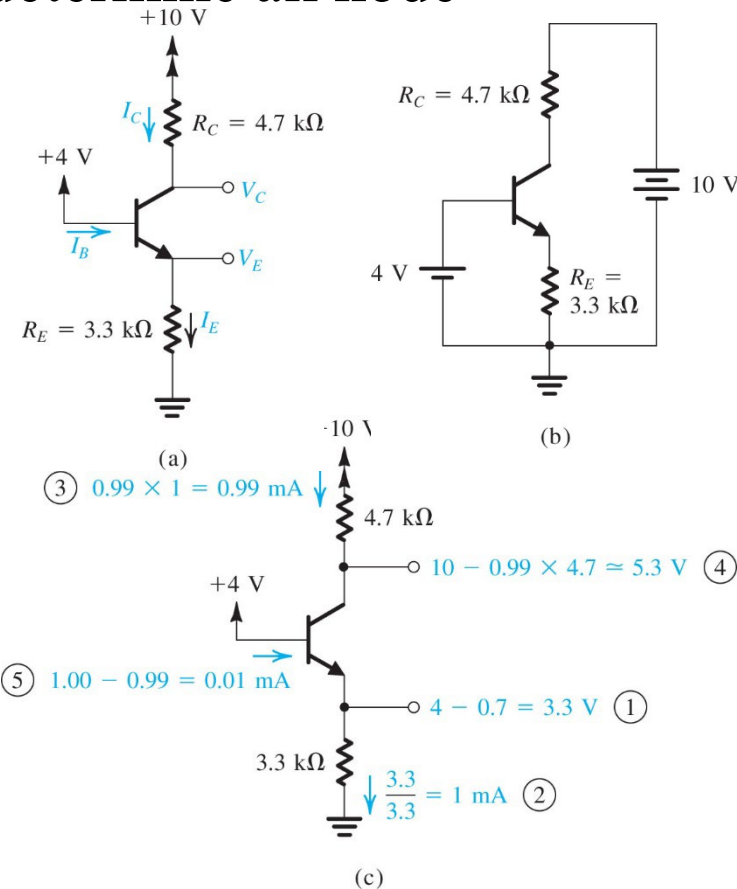

**Figure 6.23** Analysis of the circuit for Example 6.4: (a) circuit; (b) circuit redrawn to remind the reader of the convention used in this book to show connections to the dc sources; (c) analysis with the steps numbered.

# • Example 6.5

Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents. (Hint: if in saturation,  $V_{CE} \approx 0.2V$ )

1) Glancing BE is forward bias ( $V_{BE} \approx 0.7V$ ), so the transistor conducts.

$$\text{KCL1: } 6 - 0.7 - I_E R_E = 0$$

$$I_E = \frac{5.3}{R_E} = 1.6mA$$

2) Assume in active mode.

$$I_C \approx I_E, V_C = 10 - I_C R_C = 10 - 1.6 \times 4.7 = 2.48V$$

$$V_{CE} = (2.48 - 5.3) < 0.3V, \text{ the assumption is incorrect}$$

3) So reassume in saturation mode ( $V_{CE} \approx 0.2V$ )


$$\text{KCL2: } 10 - I_C \times 4.7 - 0.2 - I_E \times 3.3 = 0$$

$$\text{Since } I_E = 1.6mA \text{ (won't change), } I_C = \frac{10 - 5.5}{4.7} = 0.96mA$$

$$I_B = I_E - I_C = 1.6 - 0.96 = 0.64mA$$

$$\text{The force } \beta \text{ is } \beta_{forced} = \frac{I_C}{I_B} = 1.5$$

$$V_E = I_E \times 3.3 = 5.3 \text{ V So } V_C = V_E + 0.2 = 5.5V$$

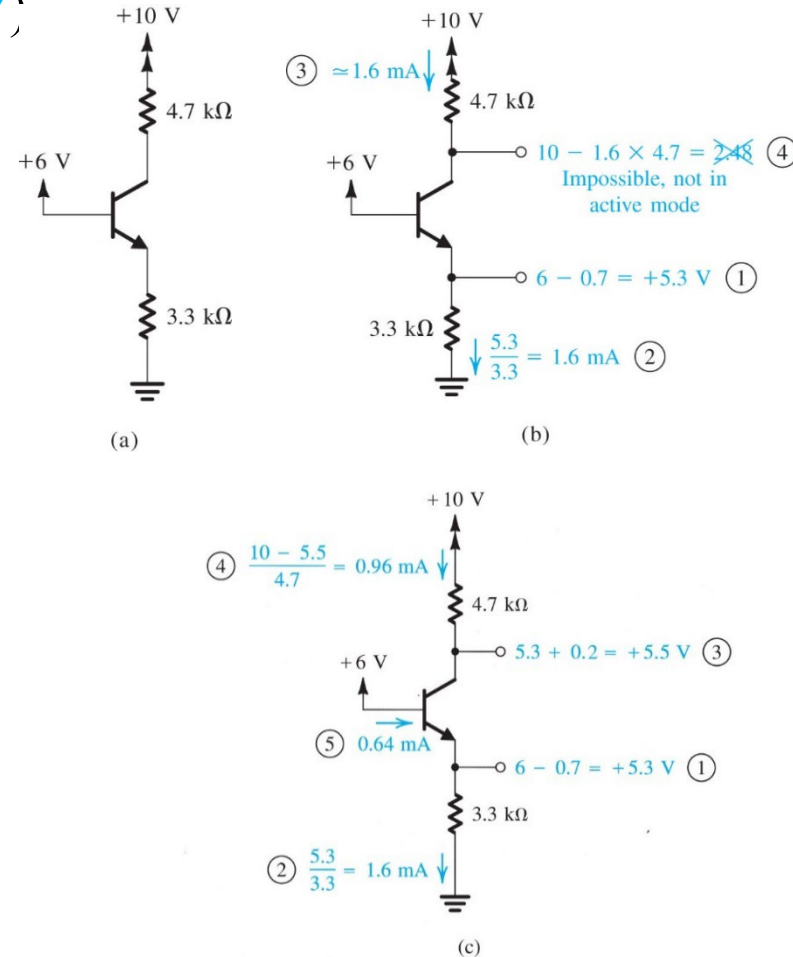

**Figure 6.24** Analysis of the circuit for Example 6.5. Note that the circled numbers indicate the order of the analysis steps.

## • Example 6.6


Analyze this circuit to determine all node voltages and branch currents.

Since the base is directly connected to ground and emitter is connected to ground through  $R_E$ , the BE cannot conduct and  $I_E = 0$

So the transistor is cutoff.

Thus,  $I_C = I_B = I_E = 0$

$V_C = 10V, V_B = V_E = 0$

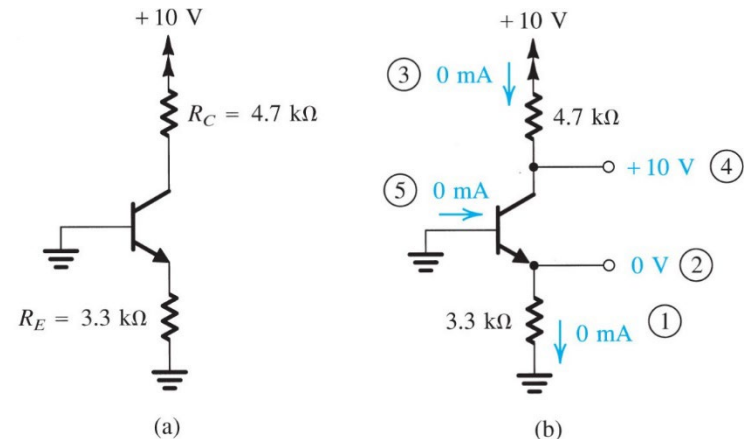

**Figure 6.25** Example 6.6: (a) circuit; (b) analysis, with the order of the analysis steps indicated by circled numbers.

# • Example 6.7

Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents.

1) Glancing EB is forward bias ( $V_{EB} \approx 0.7V$ ), so the transistor conducts.

$$\text{KCL1: } 10 - I_E R_E - 0.7 = 0$$

$$I_E = \frac{9.3}{R_E} = 4.65 \text{ mA}$$

2) Assume in active mode.

$$I_C = \alpha I_E = \frac{\beta}{1 + \beta} I_E = 0.99 \times 4.65 = 4.6 \text{ mA}$$

$$V_C = -10 + I_C R_C = -10V + 4.6 \times 1 = -5.4V$$

So  $V_{EC} = 6.1V > 0.3V$ , in active mode.

$$I_B = \frac{I_C}{\beta} = \frac{4.6}{100} = 0.046 \text{ mA}$$

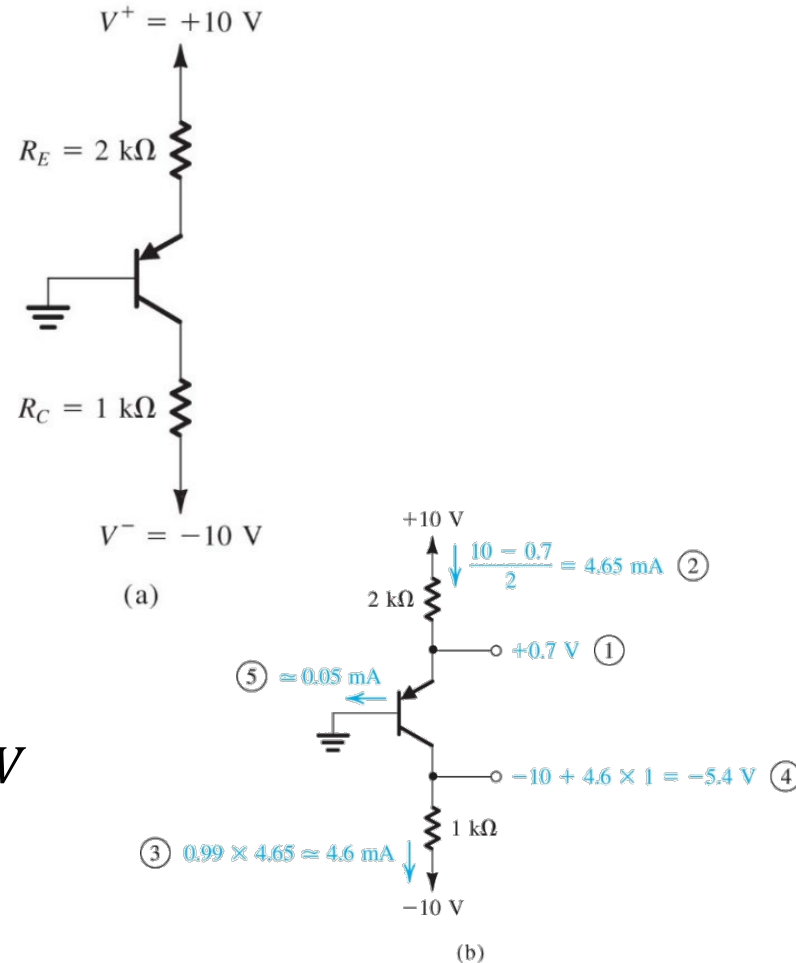


Figure 6.26 Example 6.7: (a) circuit; (b) analysis, with the steps indicated by circled numbers

# • Example 6.8

Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents.

1) Glancing BE is forward bias ( $V_{BE} \approx 0.7V$ ),  
so the transistor conducts.

$$\text{KCL1: } 5 - I_B R_B - 0.7 = 0$$

$$I_B \approx \frac{4.3}{R_B} = 0.043 \text{ mA}$$

2) Assume in active mode.

$$I_C = \beta I_B = 4.3 \text{ mA}$$

$$V_C = 10V - I_C R_C = 10 - 4.3 \times 2 = 1.4V$$

$V_{CE} = 1.4V > 0.3V$ , in active mode.

$$I_E = I_C + I_B = 4.343 \text{ mA} \approx 4.3 \text{ mA}$$

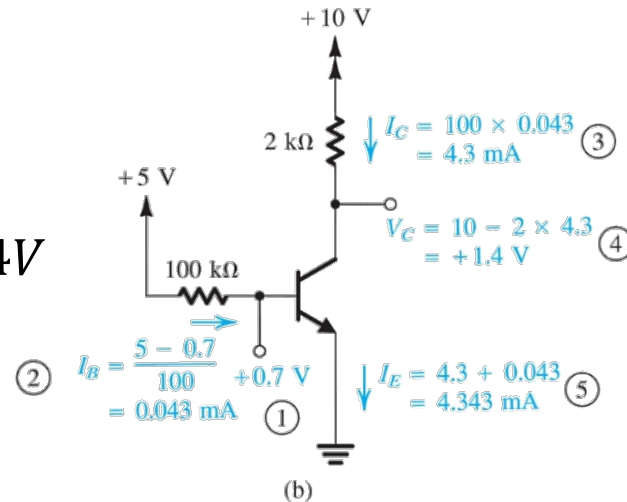
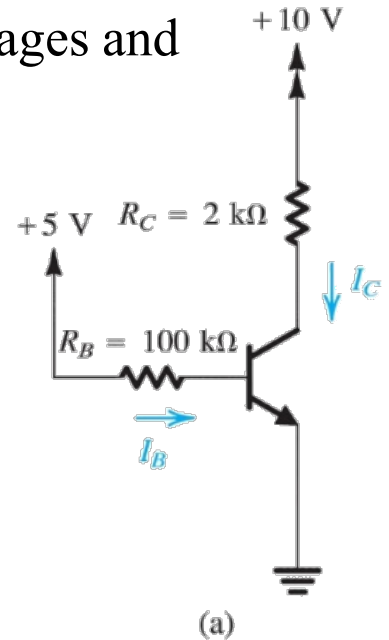


Figure 6.27 Example 6.8: (a) circuit; (b) analysis, with the steps indicated by the circled numbers.

# • Example 6.9

Assume  $\beta = 30$ , analyze this circuit to determine all node voltages and branch currents. (Hint: if in saturation,  $V_{CE} \approx 0.2V$ )

1) Glancing EB is forward bias ( $V_{EB} \approx 0.7V$ ),  
so the transistor conducts.

$$\text{KCL1: } 5 = I_B \times 10 + I_E \times 1 + 0.7$$

$$I_E = 4.3 - I_B \times 10$$

2) Assume in active mode.

$$I_E = (\beta + 1)I_B = 31I_B$$


$$\text{Thus } I_B = 0.105mA \quad I_E = 3.255mA$$

$$I_C = \beta I_B = 30 \times 0.105 = 3.15mA$$

$$V_B = I_B \times 10 = 1.05V \quad V_E = V_B + 0.7 = 1.75V$$

$$V_C = -5 + I_C R_C = -5 + 3.15 \times 10 = 26.5V$$

Since  $V_{EC} < 0.3V$ , so must be in saturation mode.

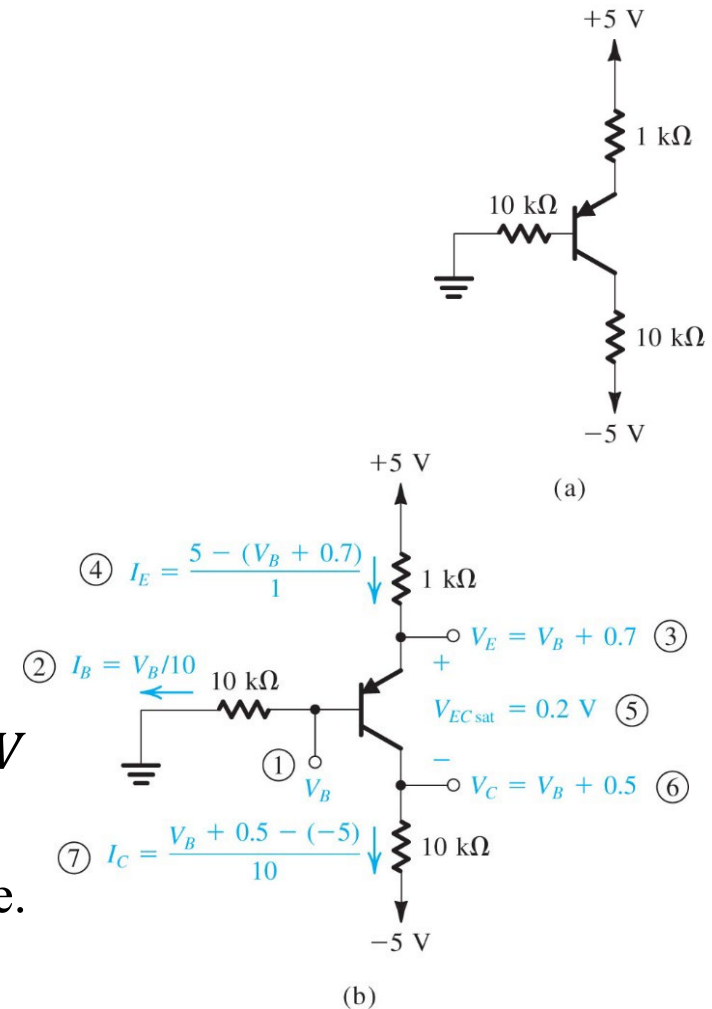

**Figure 6.28** Example 6.9: (a) circuit; (b) analysis with steps numbered.

## • Example 6.9 Cont.

Assume  $\beta = 30$ , analyze this circuit to determine all node voltages and branch currents. (Hint: if in saturation,  $V_{CE} \approx 0.2V$ )

3) So reassume in saturation mode ( $V_{EC} \approx 0.2V$ )

$$\text{KCL1: } 5 - I_E \times 1 - 0.7 - I_B \times 10 = 0 \quad \textcircled{1}$$

$$\text{KCL2: } 5 - I_E \times 1 - 0.2 - I_C \times 10 - (-5) = 0 \quad \textcircled{2}$$

Since  $I_E = I_B + I_C$ ,  $\textcircled{3}$ .

$$I_B = 0.31\text{mA}, I_C = 0.86\text{mA}, I_E = 1.17\text{mA}$$

$$V_E = 5 - I_E \times 1 = 3.83V,$$

$$V_C = -5 + I_C \times 10 = 3.63V,$$

$$V_B = I_B \times 10 = 3.13V$$

From which we can see the transistor is saturation,

$$\beta_{forced} = \frac{I_C}{I_B} = 2.8 \text{ which is much smaller than } \beta$$

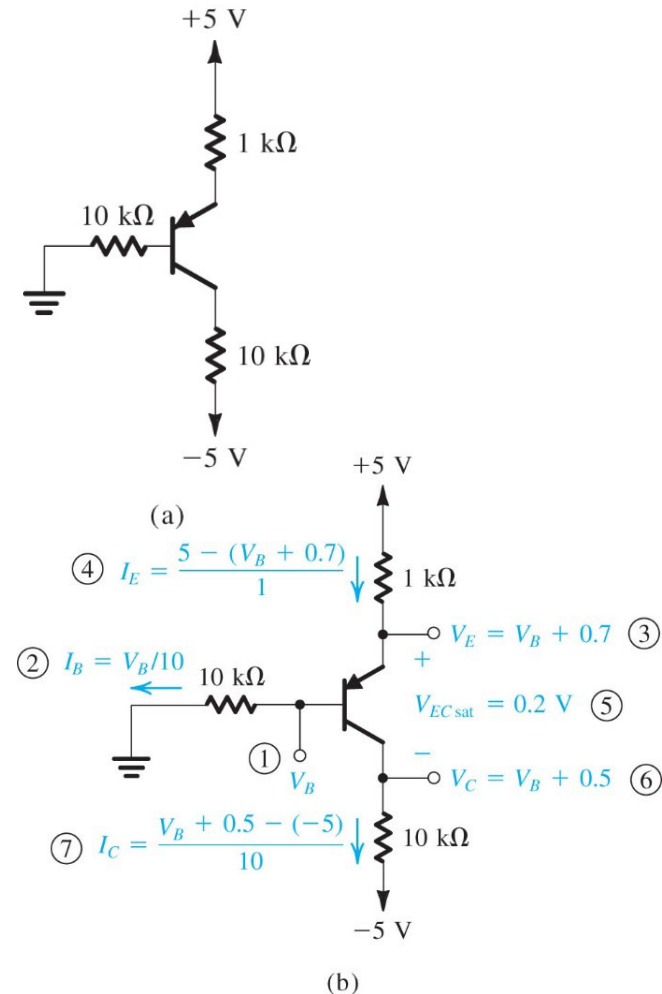


Figure 6.28 Example 6.9: (a) circuit; (b) analysis with steps numbered.

# • Example 6.10

Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents.

Thévenin Equivalent Circuits (a)→(b)

$$V_{BB} = 15V \times \frac{R_{B2}}{R_{B2}+R_{B1}} = 5V \quad R_{BB} = R_{B2} \parallel R_{B1} = 33.3k\Omega$$

1) Glancing BE is forward bias ( $V_{BE} \approx 0.7V$ ),  
so the transistor conducts.

$$\text{KCL1: } 5 - I_B \times 33.3 - 0.7 - I_E \times 3 = 0$$


$$I_E = \frac{4.3 - I_B \times 33.3}{3} \quad \textcircled{1}$$

2) Assume in active mode.  $I_E = (\beta + 1)I_B = 101I_B \quad \textcircled{2}$

$$\text{Thus, } \frac{4.3 - I_B \times 33.3}{3} = 101I_B \Rightarrow I_B = 0.0128mA,$$

$$I_E = 101 \times I_B = 1.29mA,$$

$$I_C = I_E = I_B = 1.28mA$$

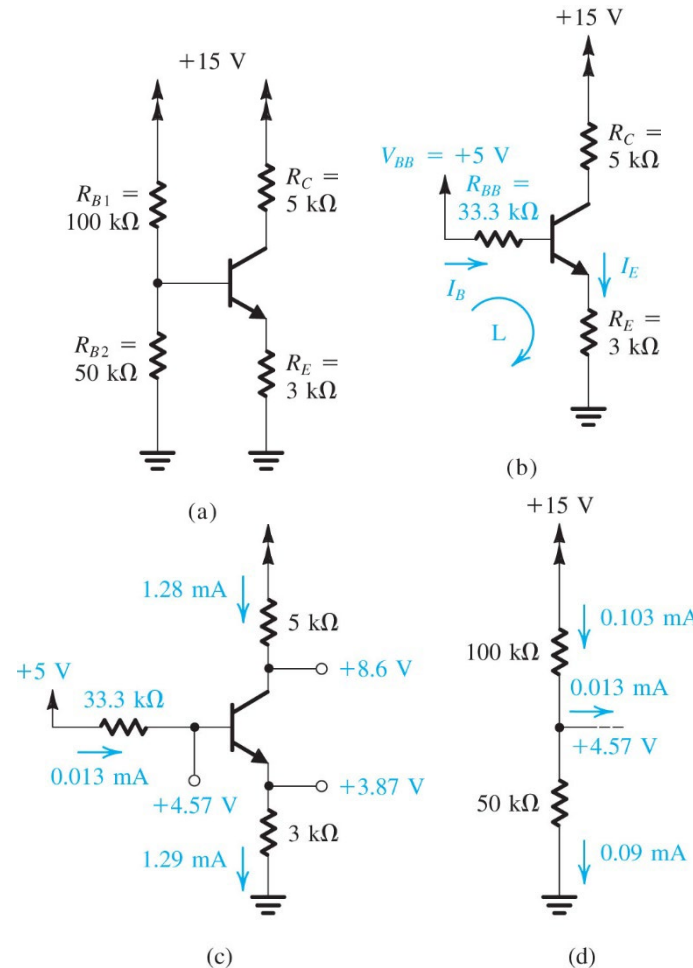

# • Example 6.10


Assume  $\beta = 100$ , analyze this circuit to determine all node voltages and branch currents.

$$V_B = 5 - I_C \times 33.33 = 4.57V,$$

$$V_E = V_B - 0.7 = 3.87V,$$

$$V_C = 15V - I_C \times 5 = 8.6V$$
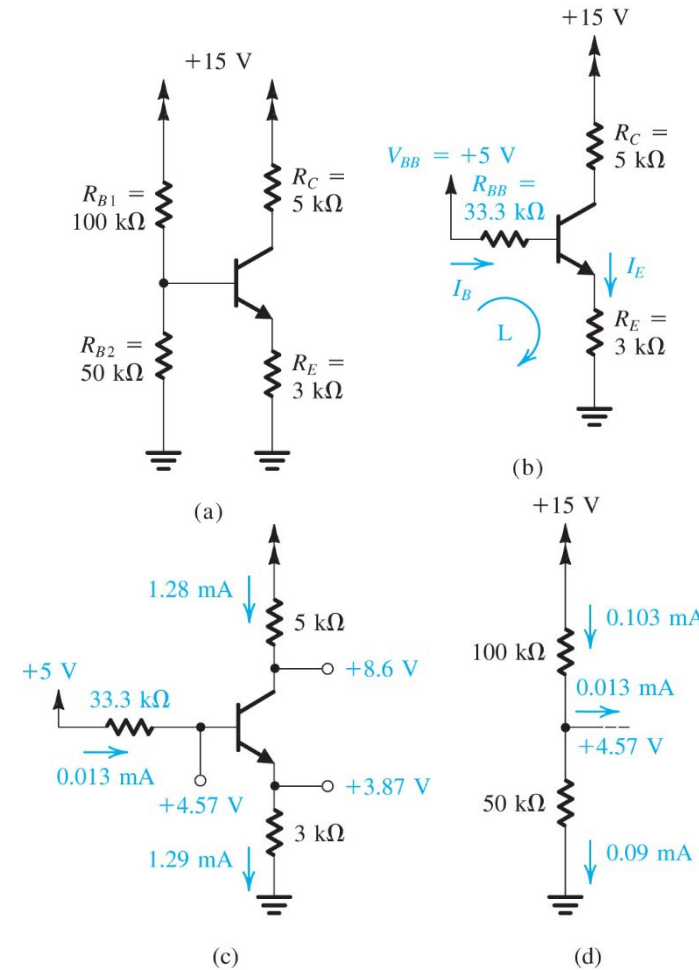
$$V_{CE} = 4.73V > 0.3V, \text{ in active region.}$$




# • Experiment 9.1

Set up the following circuit with NPN BJT (**2N3904/2N4401**).

$$V_{CC} = 5V, V_{EE} = 8V.$$

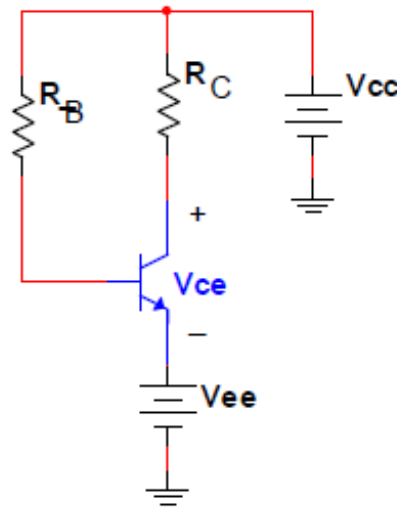Measure  $V_{CE}$ ,  $V_{BE}$ , and  $V_{CB}$ . In which region does the BJT operate for each corresponding  $R_C$  and  $R_B$ ? Briefly explain and comment your results.




$R_C$	$R_B$	$V_{CE}$	$V_{BE}$	Region
$1k\Omega$	$1k\Omega$			
$1k\Omega$	$1M\Omega$			
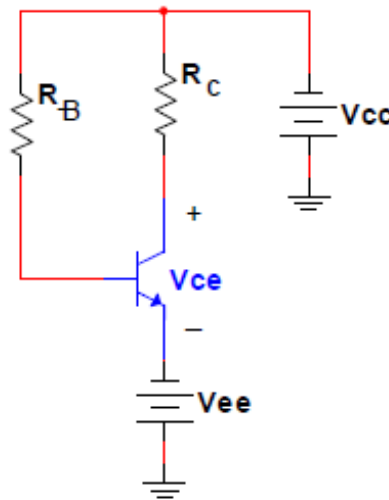
# • Experiment 9.2

$V_{CC} = -5V, V_{EE} = -8V.$

Measure  $V_{CE}, V_{BE},$  and  $V_{CB}.$  In which region does the BJT operate for each corresponding  $R_C$  and  $R_B?$  Briefly explain and comment your results.




$R_C$	$R_B$	$V_{CE}$	$V_{BE}$	Region
$1k\Omega$	$1k\Omega$			
$1k\Omega$	$1M\Omega$			
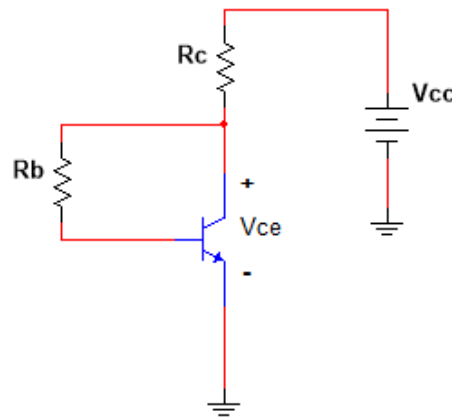
# • Experiment 9.3

$V_{CC} = 5V$ .

Measure  $V_{CE}$ ,  $V_{BE}$ , and  $V_{CB}$ . In which region does the BJT operate for each corresponding  $R_C$  and  $R_B$ ? Briefly explain and comment your results.




$R_C$	$R_B$	$V_{CE}$	$V_{BE}$	Region
$1k\Omega$	$1k\Omega$			
$1k\Omega$	$1M\Omega$			

# • Experiment 9.4

Set up the following circuit with PNP BJT (**2N3906/4403**).

$V_{ee} = 15V$  and  $V_{cc} = -15V$ .

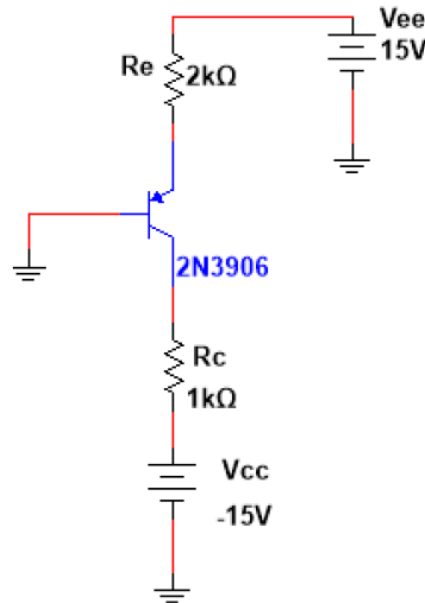Measure  $V_{EC}$ ,  $V_{EB}$ , and  $V_{BC}$ . In which region does the BJT operate for each corresponding  $R_E$  and  $R_B$ ? Briefly explain and comment your results.



$R_E$	$R_C$	$V_{EC}$	$V_{EB}$	Region
$2k\Omega$	$1k\Omega$			

# HW6

- Problems
  - PP.360, 6.48 – Current-voltage characteristics
  - PP.339, Exercice 6.22 – BJT circuits at DC #1
  - PP.339, Exercice 6.23 – BJT circuits at DC #2
  - PP.340, Exercice 6.24 – BJT circuits at DC #3
- Submission requirement:
  - Add the cover page!!!
  - [Print the HW6.pdf out and answer all the questions](#)
- Due: [TBA \(Late assignments: 40% deduction. \)](#)